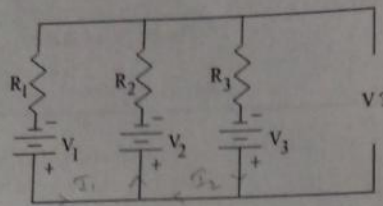




Figure 3



(a) Question number 4

4. (1 point) Identify the mathematical operation on the voltage sources achieved at the output V by the circuit shown in Figure (3a)

A. Mean of all voltages
B. Mode of all voltages

C. Median of all voltages

☒ D. None of these

5. (2 points) The horizontal and vertical sensitivity knobs of a CRO are set to 50ms/div and 4V/div respectively. If a signal, $x(t) = 8\cos(10\pi t + 30^\circ)$ V is applied at Ch-1, find the number of vertical and horizontal divisions spanned by one cycle on the screen of the CRO.

A. Number of vertical div.: 4

B. Number of horizontal div.: 4

$$-V_2 - (I_1 + I_2)R_2 - I_1R_1 + V_1 = 0$$

$$-V_3 + I_2R_3 + (I_2R_2 + I_1R_2) + V_2 = 0$$

$$V_2 + I_2R_2 = V_3 - I_2R_3 = V_1 - I_1R_1 - I_1R_2 - I_1R_2$$

$$V_3 - I_2R_3 = V_1 - I_1R_2$$

$$I_1 = \frac{V_1 - V_3 - I_2R_3}{R_2}$$

$$-V_3 + I_2R_3 + (V_1 - V_3 - I_2R_3 + I_1R_2) + V_2 = 0$$

$$\frac{V_1 \times R_1}{R_1 + \frac{R_2R_3}{R_2 + R_3}}$$

$$\frac{V_1(R_1R_2 + R_2R_3)}{R_1R_2 + R_1R_3 + R_2R_3}$$

$$\frac{V_2 \times R_2}{R_2 + \frac{R_1R_3}{R_1 + R_3}}$$



$$\omega = 10\pi$$

$$\frac{2\pi}{10\pi} = \frac{1}{5}$$

$$= 2.00 \text{ m}$$