



13. (1 point) For the circuit shown in Figure (7a), the plot V_o when the polarity of dc supply $V_m/2$ is reversed

Ans:

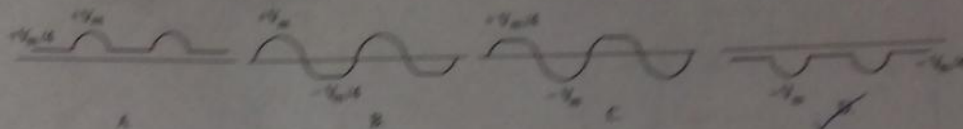


Figure 9: Answer for question 13

14. (1 point) For the circuit shown in Figure (7a), the plot V_o when the polarity of diode D is reversed

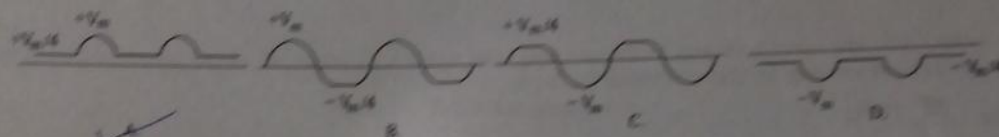


Figure 10: Answer for question 14

15. (1 point) For the circuit shown in Figure (7b), determine the average value of the current through the load resistor


A. 0

B. 0.79 mA


☒ C. 1.59 mA

D. 3.18 mA

Figure 11

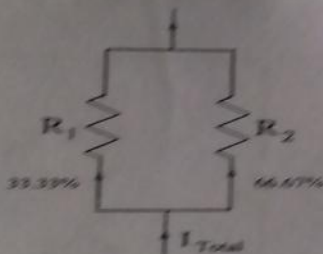

(a) Question number 16

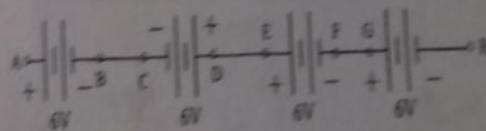

(b) Question number 17

16. (1 point) For the circuit shown in Figure (11a), the current through the resistors are 33.33% and 66.67% of I_{Total} , approximately. The relation between R_1 and R_2 is

A. $2R_1 = R_2$

B. $3R_1 = 2R_2$

☒ C. $R_1 = 2R_2$

D. $2R_1 = 3R_2$

17. (2 points) For the circuit shown in Figure (11b), what is the potential difference between the following nodes

A. AH = 12V

B. CG = 0V

C. FB = 0V

D. FA = -6V

$$\frac{R_1}{R_1 + R_2} = \frac{1}{2}$$

$$2R_2 = 3R_1$$