



<u>Regular Session & Group:</u>	<u>Wednesday, Afternoon. (L8)</u>
<u>EXPT. NO:</u>	<u>FOUR (4)</u>
<u>DATE OF EXPT:</u>	<u>10/2/2016</u>
<u>STUDENT -1:</u>	<u>K.Y. Ashok (150107027)</u>
<u>STUDENT -2:</u>	<u>K. Indramani (150107028)</u>

③
for


Exp-4:

re-observation Reading :-



- A) Half-Wave Rectifier without filter;

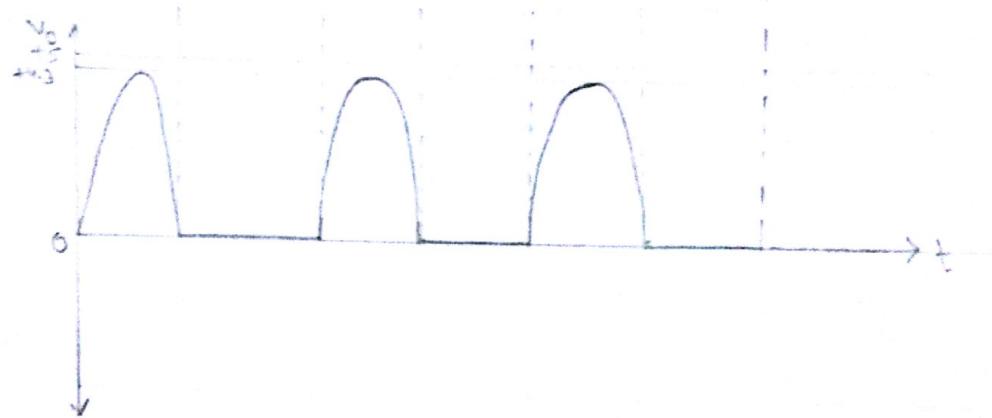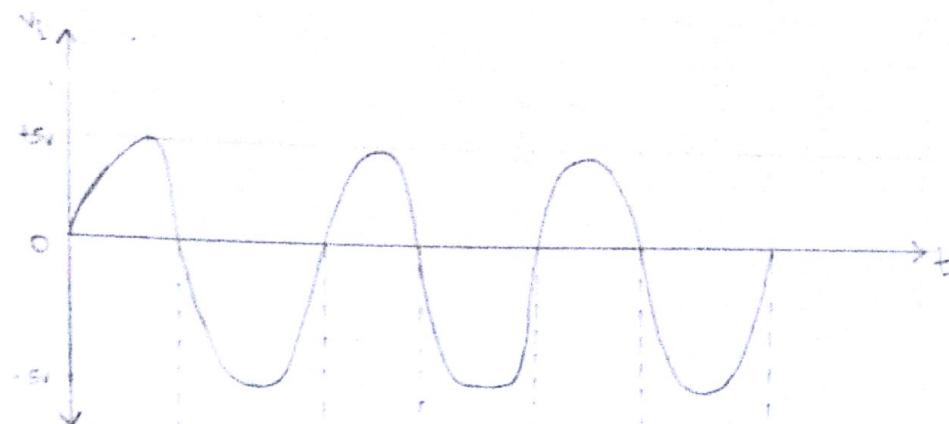

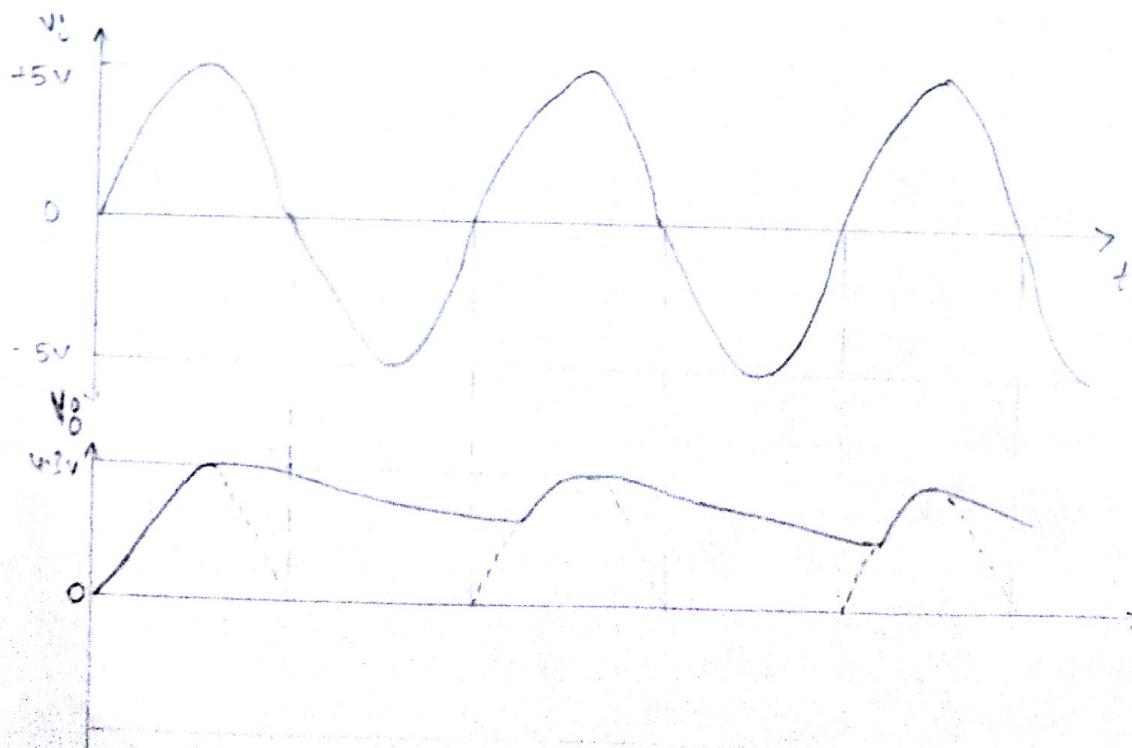- B) Half-Wave Rectifier with Capacitor Filter;





c) Clipping circuit: Positive clipper

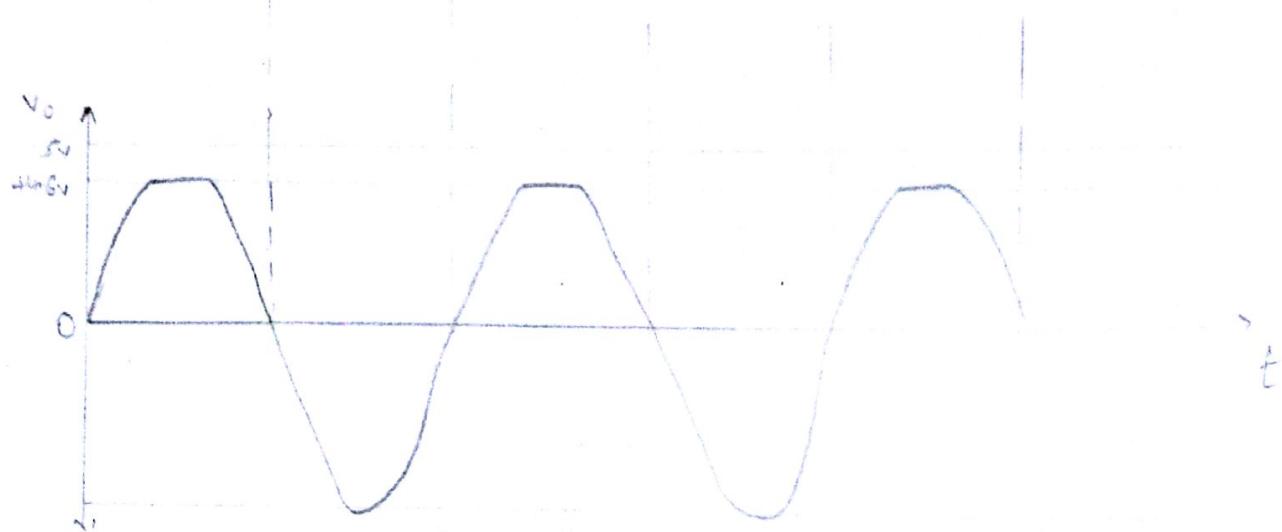
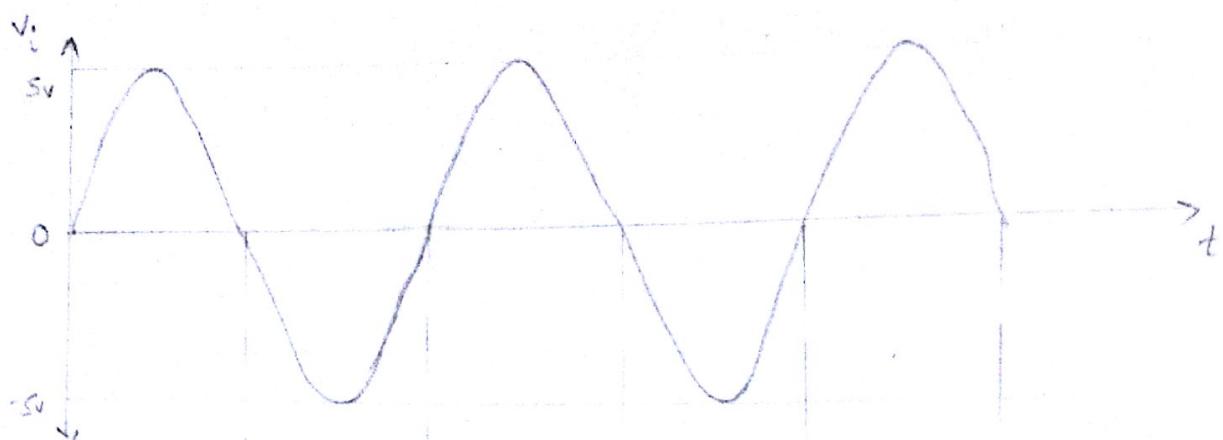


~~Part-B~~ With 56 Ω Resistance in series


a) With $R_L = 2.2\text{k}\Omega$

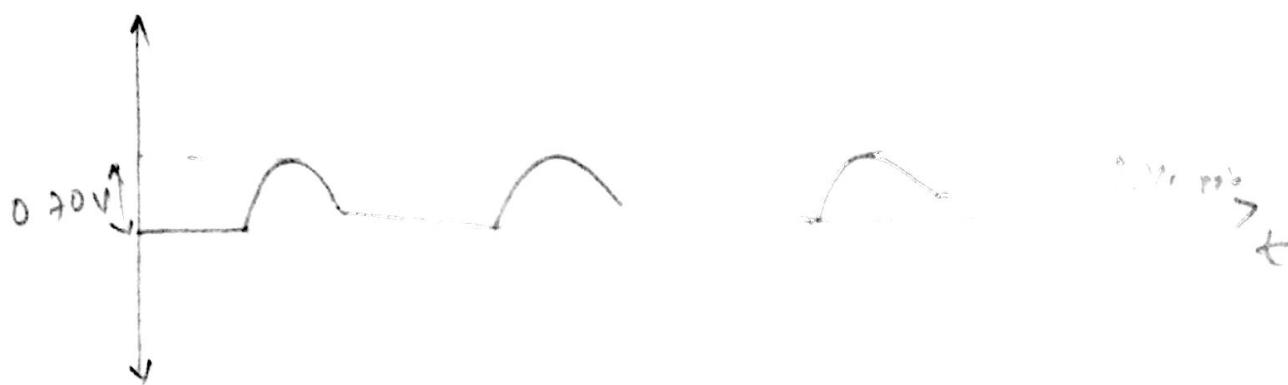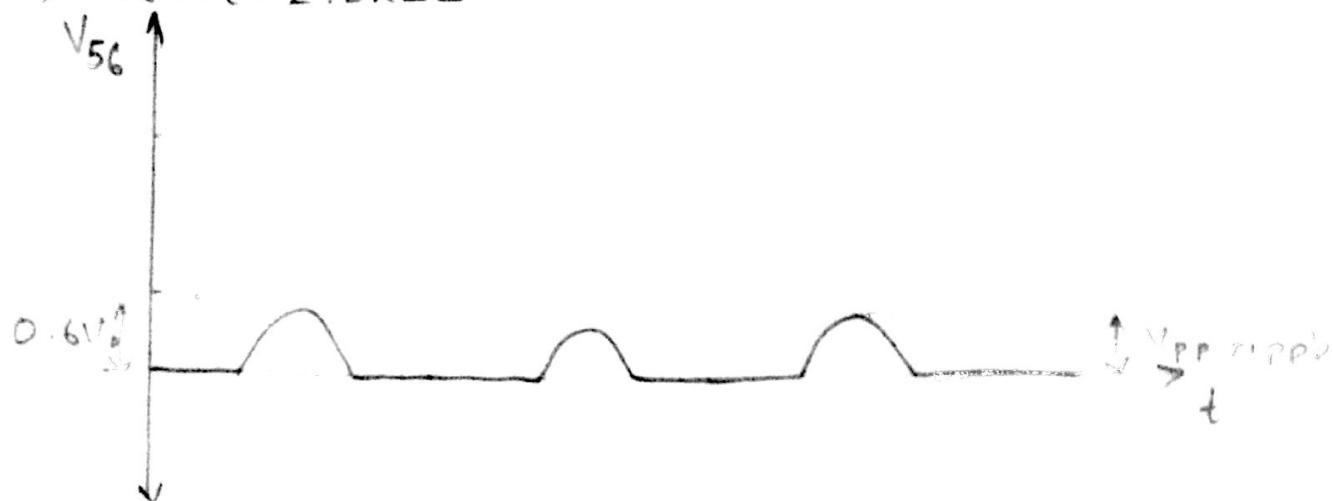


b) With $R_L = 1\text{k}\Omega$:

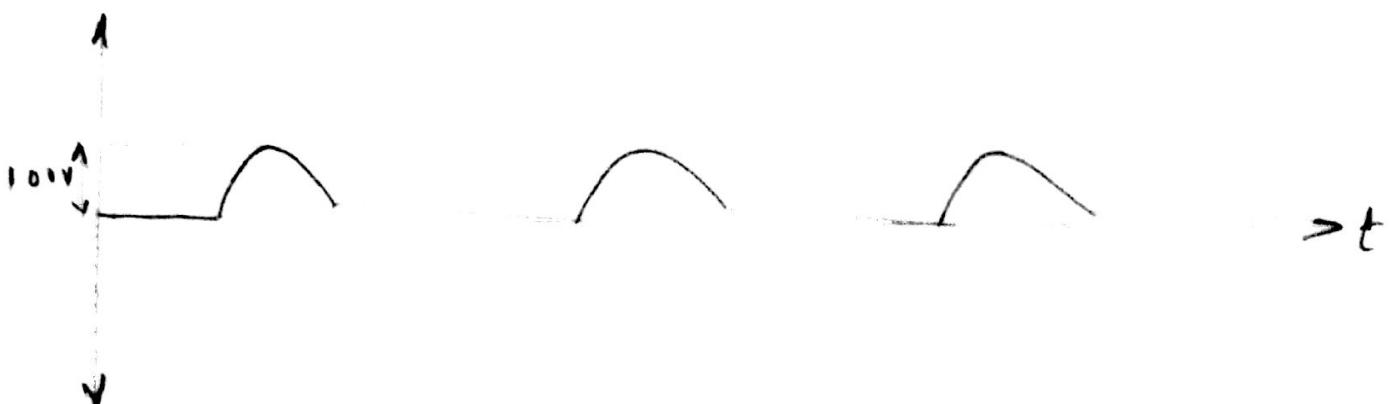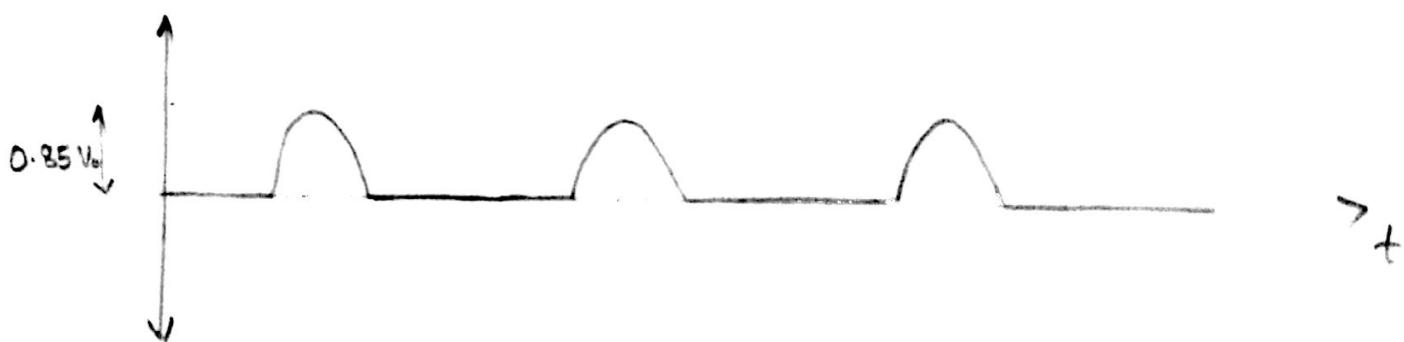

c) With $R_L = 4.2 \text{ k}\Omega$

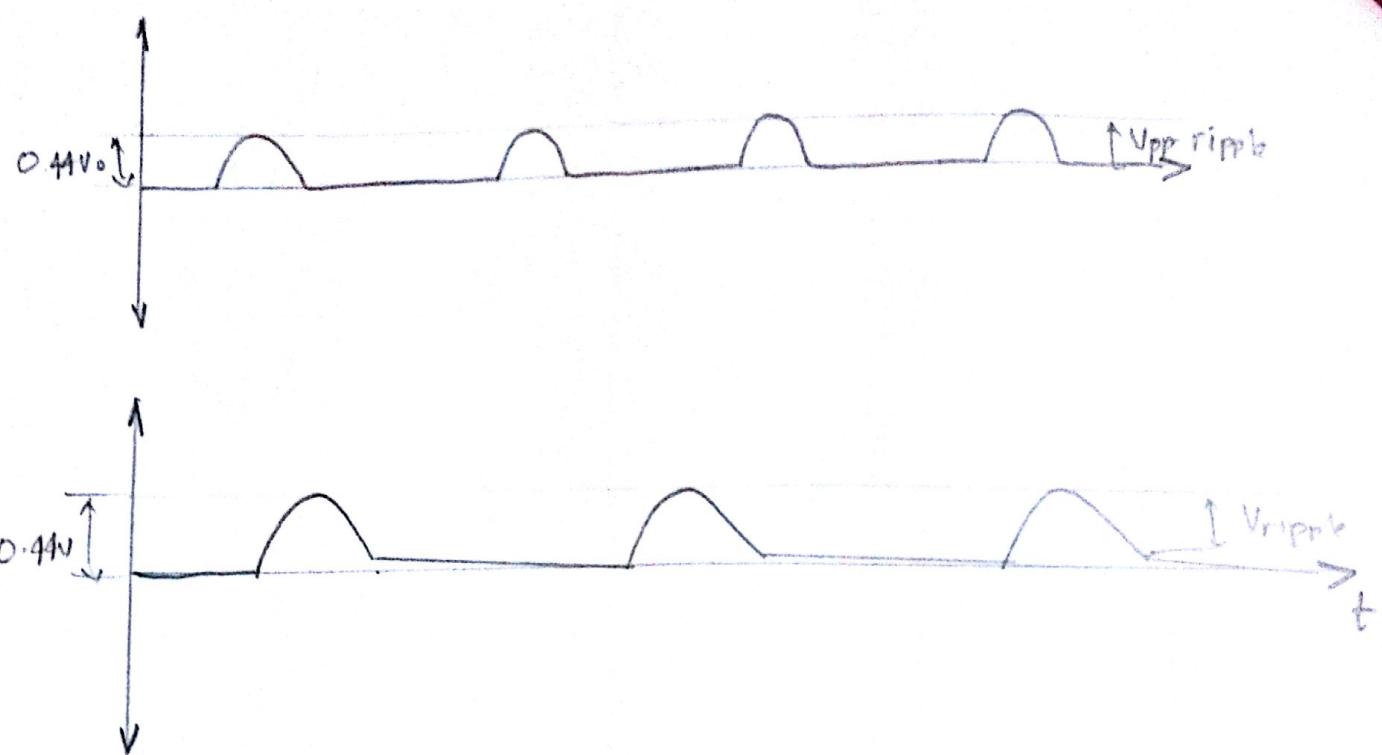


PART - C

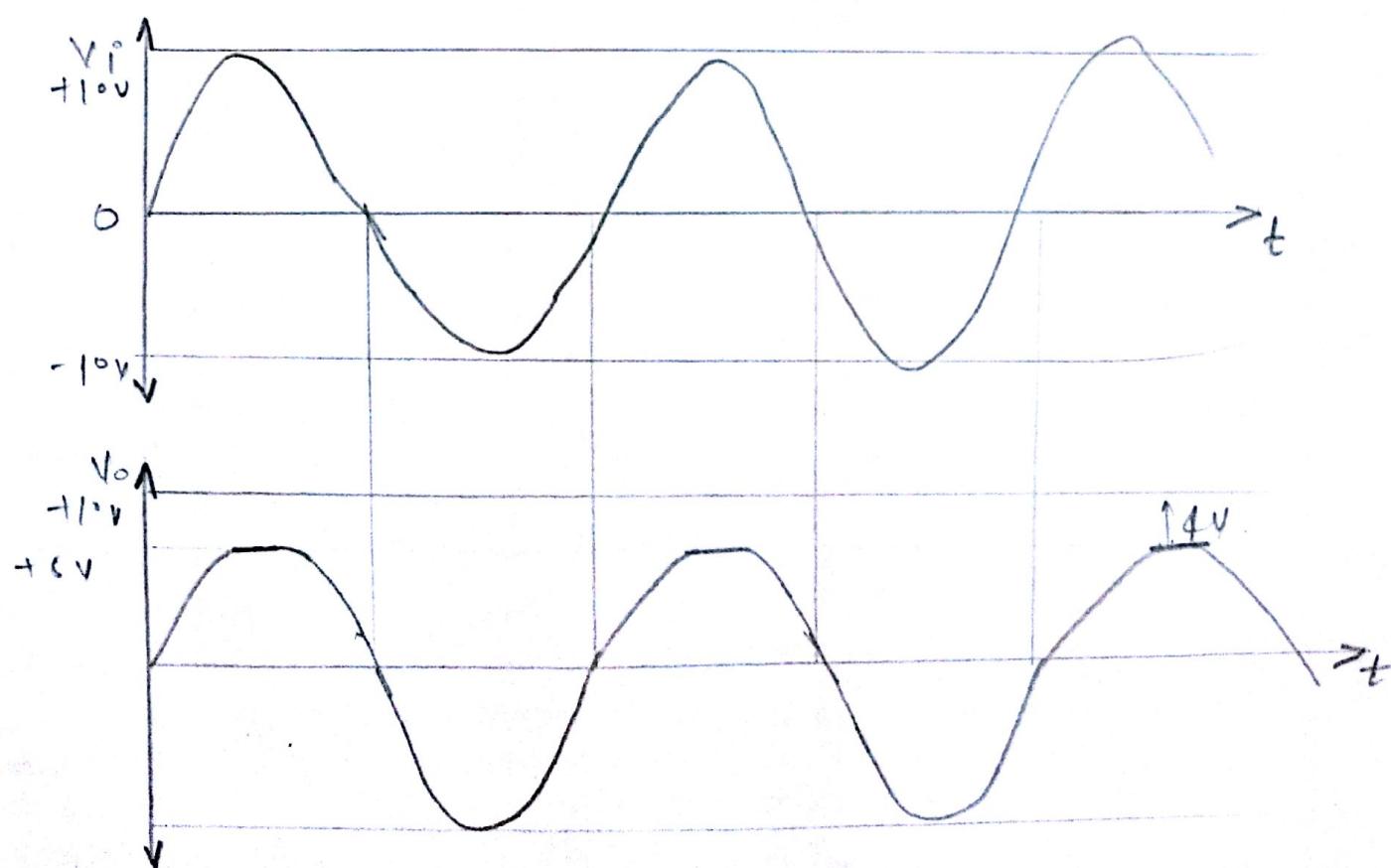

→ Design and analysis of Half wave rectifier and clipping circuits.


Circuit Diagrams →

PART A:

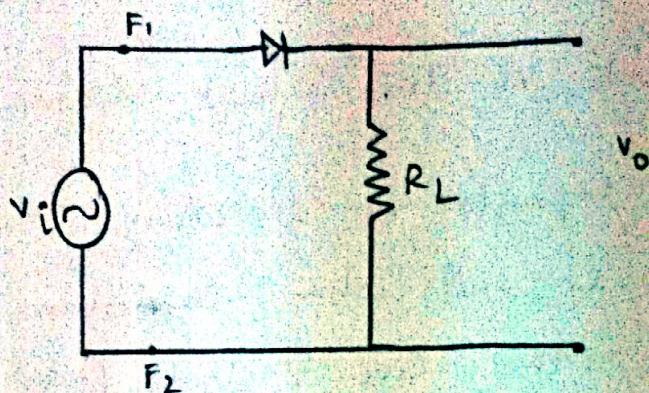


$$R_L = 2.2 \text{ k}\Omega$$

PART B:

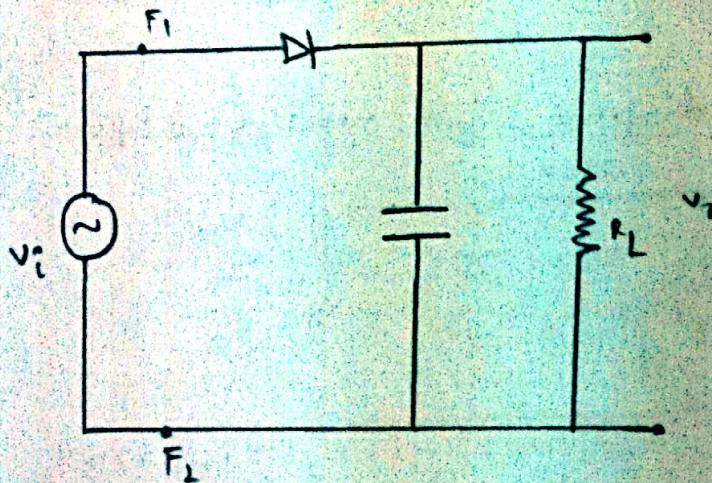


$$C = 22 \mu\text{F}$$
$$R_L = 2.2 \text{ k}\Omega, 1 \text{ k}\Omega, 4.7 \text{ k}\Omega$$

Half Wave rectifier with;

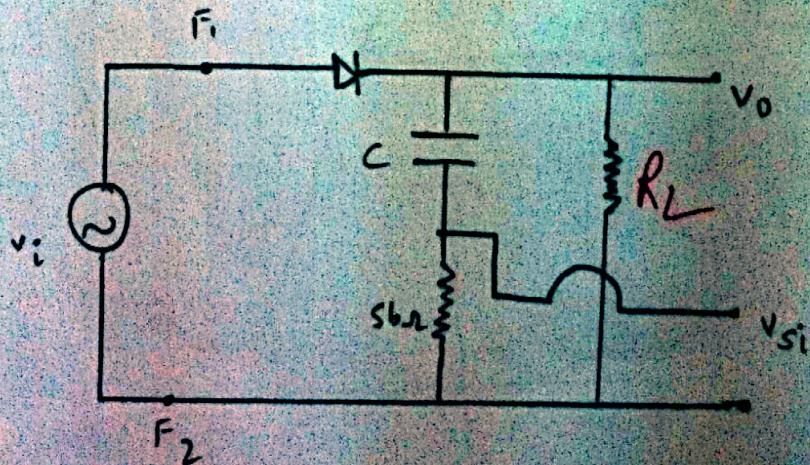

PART C:

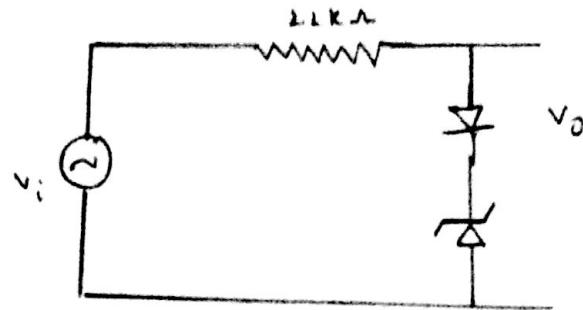


Positive clipper.

Q.1) If we look at the circuit diagram;


when ever .Capacitor is in charging mode

Current is I_1 and when .Capacitor is discharging
Current in .the Circuit is I_2 (most of the time).

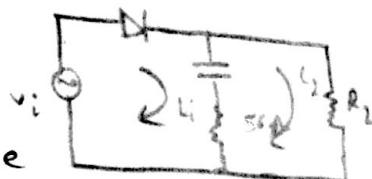
We will see that Capacitor is in charging mode
only for short interval of time.



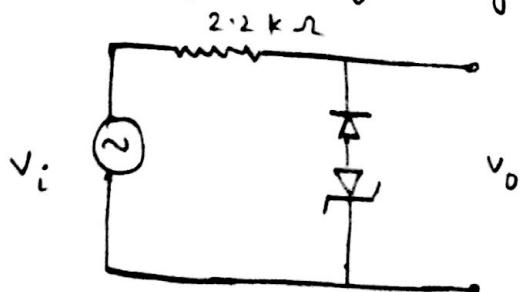Q.2) Circuit diagram for negative clipper;



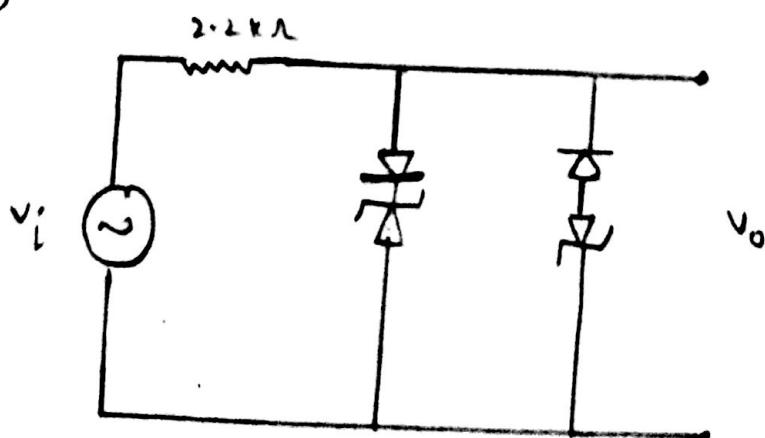Circuit diagram for Combined positive and negative
clipper;



EXPERIMENTAL OBSERVATIONS:

Setting input voltage at 10V peak to peak and 500Hz and connecting it to Half Wave rectifier circuit. The output obtained on the oscilloscope is similar to the output expected but the peak of the output is about 4.2V. Hence the voltage drop across diode comes to be 2V. which may be due to behaviour of semiconductors devices at lab's temperature.

→ When we connected a capacitor filter in the circuit diagram, we get the plot similar to expected graph and the ripple voltage was changing with changing of load resistances.

$$\text{At } R_L = 2.2 \text{ k}\Omega; V_{\text{ripple}} = 0.2 \text{ V}$$

$$\text{At } R_L = 4.7 \text{ k}\Omega; V_{\text{ripple}} = 0.1 \text{ V}$$

$$\text{At } R_L = 1 \text{ k}\Omega; V_{\text{ripple}} = 0.3 \text{ V}$$

We observed that as R_L increases; V_{ripple} also decreases.

→ Actually the ripple is amount of discharging of capacitor in the equal to time period of input frequency. As it is constant for all resistances. So, remaining factors are R_L and C (i.e. time constant). So; when R_L increases, $R_L C$ increases i.e. time constant of capacitor increases.

rather . Call it. And we know that as time const. Increases . decay amount in a given time increases.

→ We found that;

$$V_{56\Omega} ; \cancel{0.1k\Omega} = R_L$$

So current I_C through 56Ω resistor = $0.85 V_0$

→ In clipper circuit;

We know that when ever V_i is greater than $4.6V$; the diode is forward biased and Hence $V_o = 4.6V$. otherwise $V_o = V_i$.

→ In our case of experiment, we got the value $4.3V$ rather than $4.6V$. This may be due to some difference in values provided for us and actual values of voltage drop across diode and Zener diode at the given conditions as we got some differences in case of Half Wave rectifiers as well.

CONCLUSIONS:

- 1) Half Wave rectifier is used to 'choose' (or) correct one section of the wave .. since we wanted the +ve half, we selected that (diode forward biased) and the (-ve) half was discarded (diode reverted biased).
- 2) In order to minimise oscillations a capacitor was used in the rectifier circuit.

The resistance values used in AC rectifier should be high.


- 4) The study and effect of different components on the rectifier circuit and differ circuits was performed.

PRECAUTIONS:

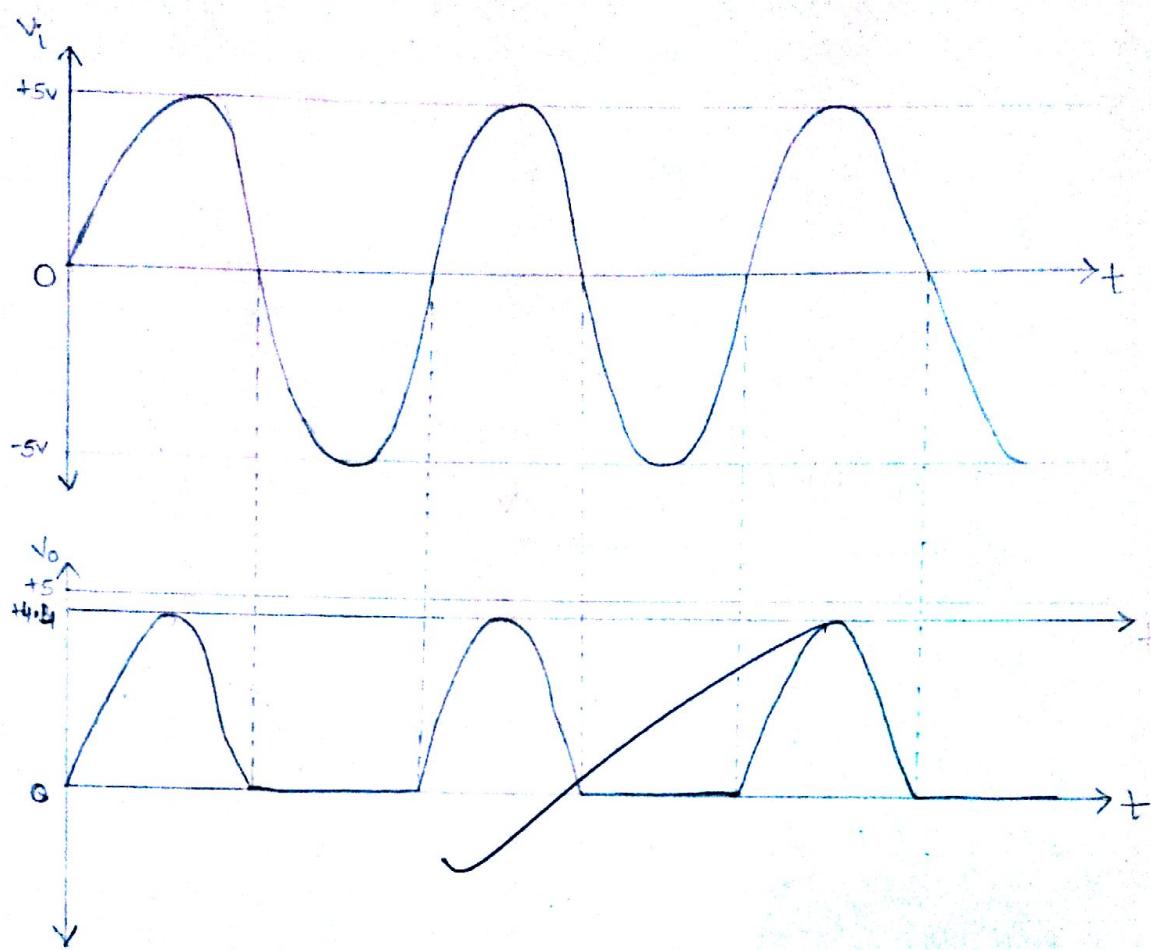- 1) Confirm the polarity of the diode.
- 2) Connect the capacitor with correct polarity as capacitor is electrolytic. It will be damaged if connected with incorrect polarity.
- 3) Keep ground terminal of Oscilloscope, probe and function generator connected together throughout the experiment.
- 4) In the Oscilloscope; for higher precision; increase vertical sensitivity while measuring small voltage (ripple voltage).

SOLUTIONS:-


PART-A
Half-Wave Rectifier without filter;



PART-B

B) Half-Wave Rectifier with Capacitor Filter;


(a) $V_i \wedge V_o$

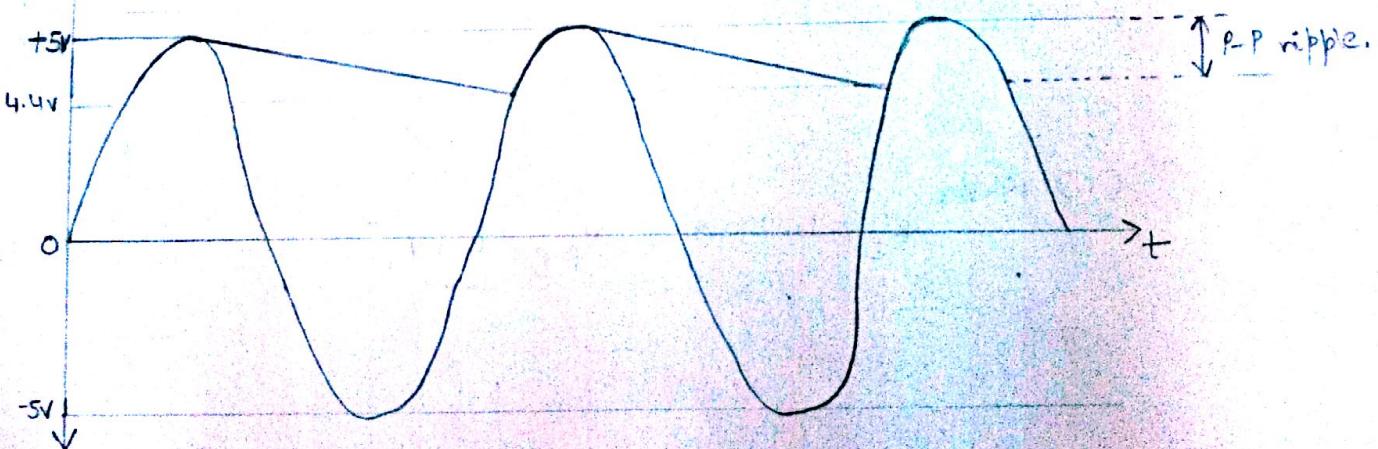

(a) With $R_L = 2.2\text{k}\Omega$ and $C = 22\mu\text{F}$;


$$\underline{\underline{V_{P-P} \text{ ripple} = 0.2\text{V}}}$$

(b)

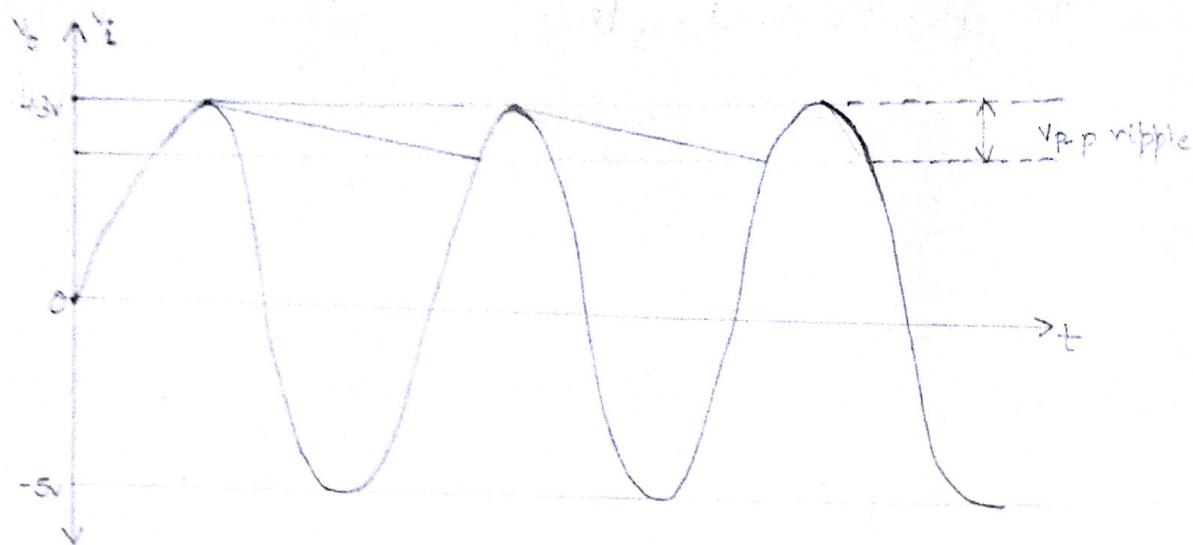

(b) With $R_L = 1 \text{ k}\Omega$; $\underline{v_{p-p} = 0.3V}$.

(c)

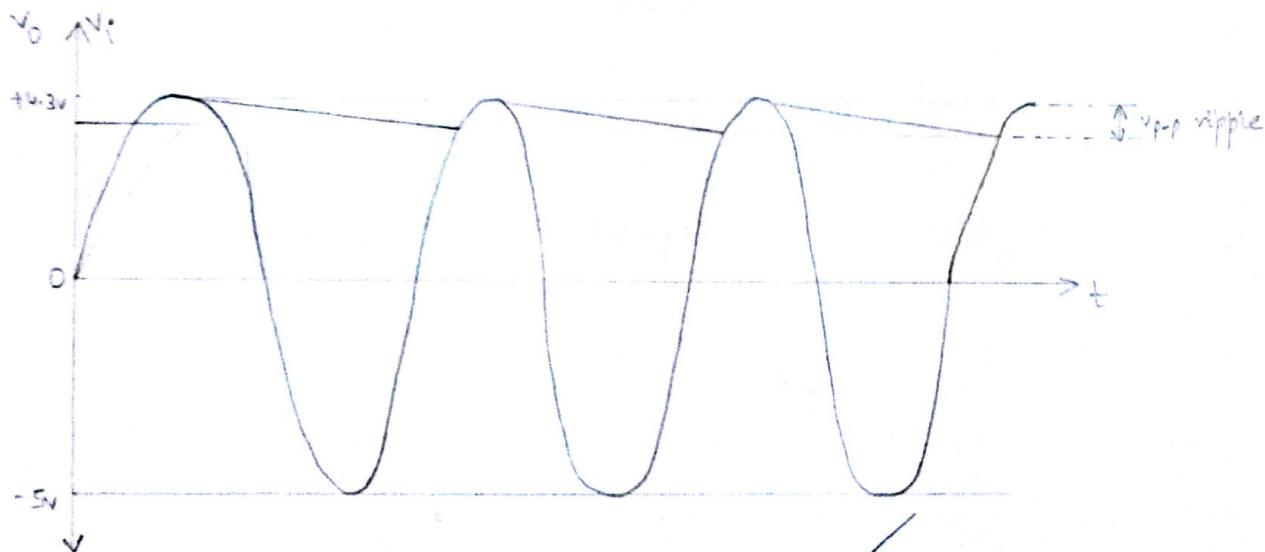



(c) with

$R_L = 4.7 \text{ k}\Omega$; $\underline{v_{p-p} = 0.1V}$.



A-B:

With $V_{56 \text{ m}}$


a) with $R_L = 2.2 \text{ k}\Omega$;

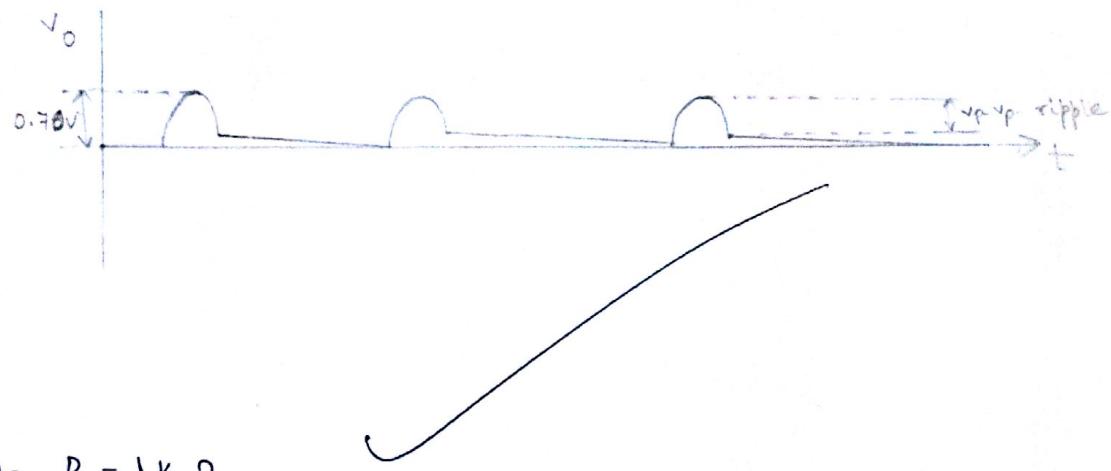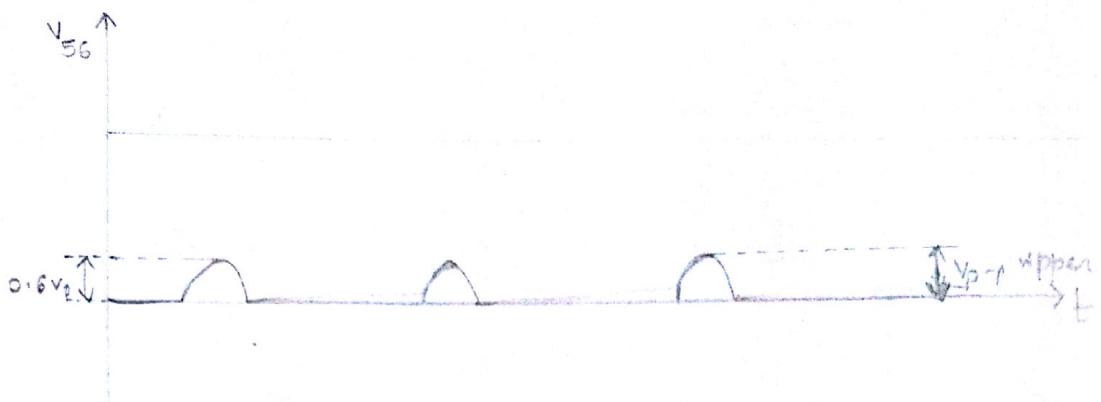


b) with $R_2 = 1 \text{ k}\Omega$;

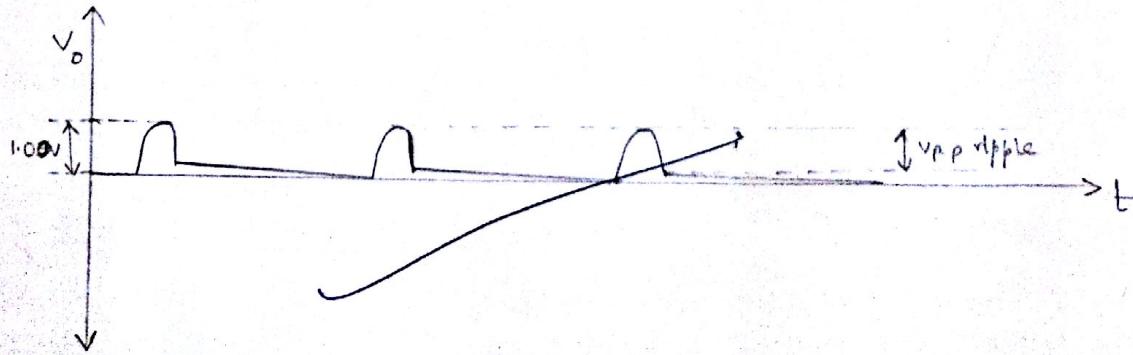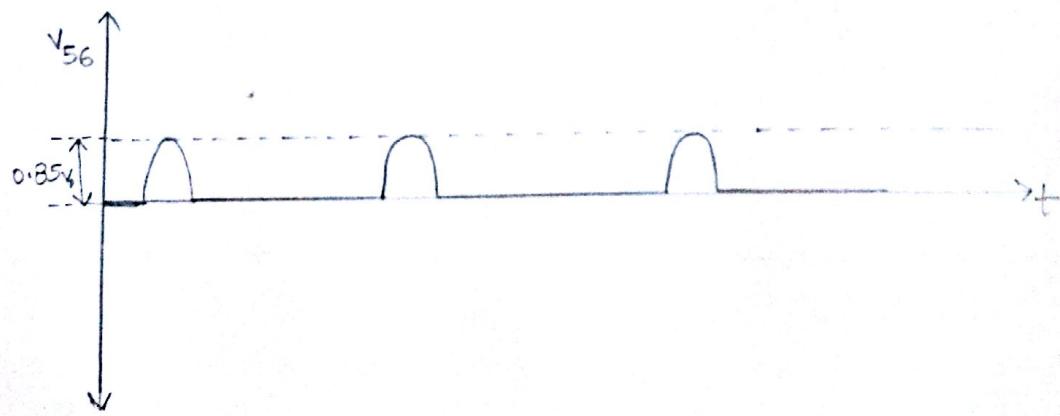

c) with $R_L = 4.7 \text{ k}\Omega$

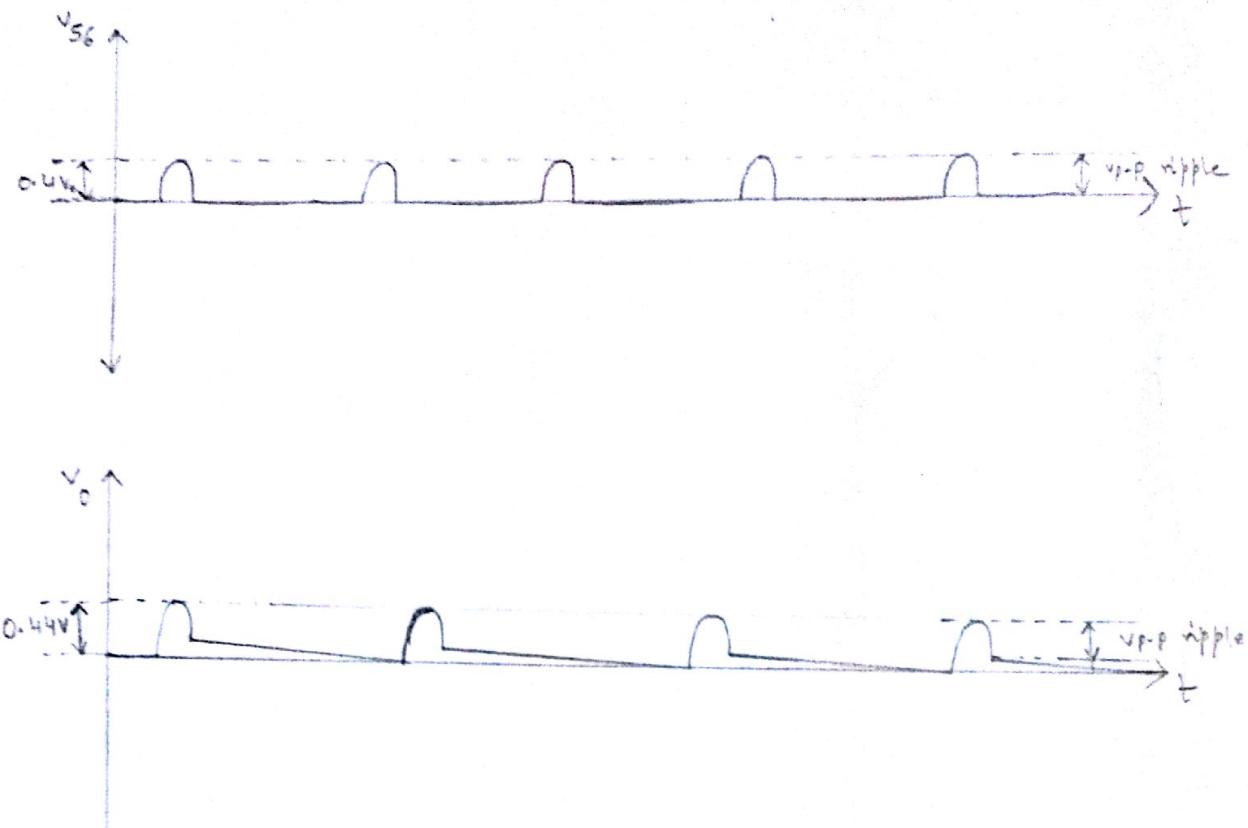


PART C:-

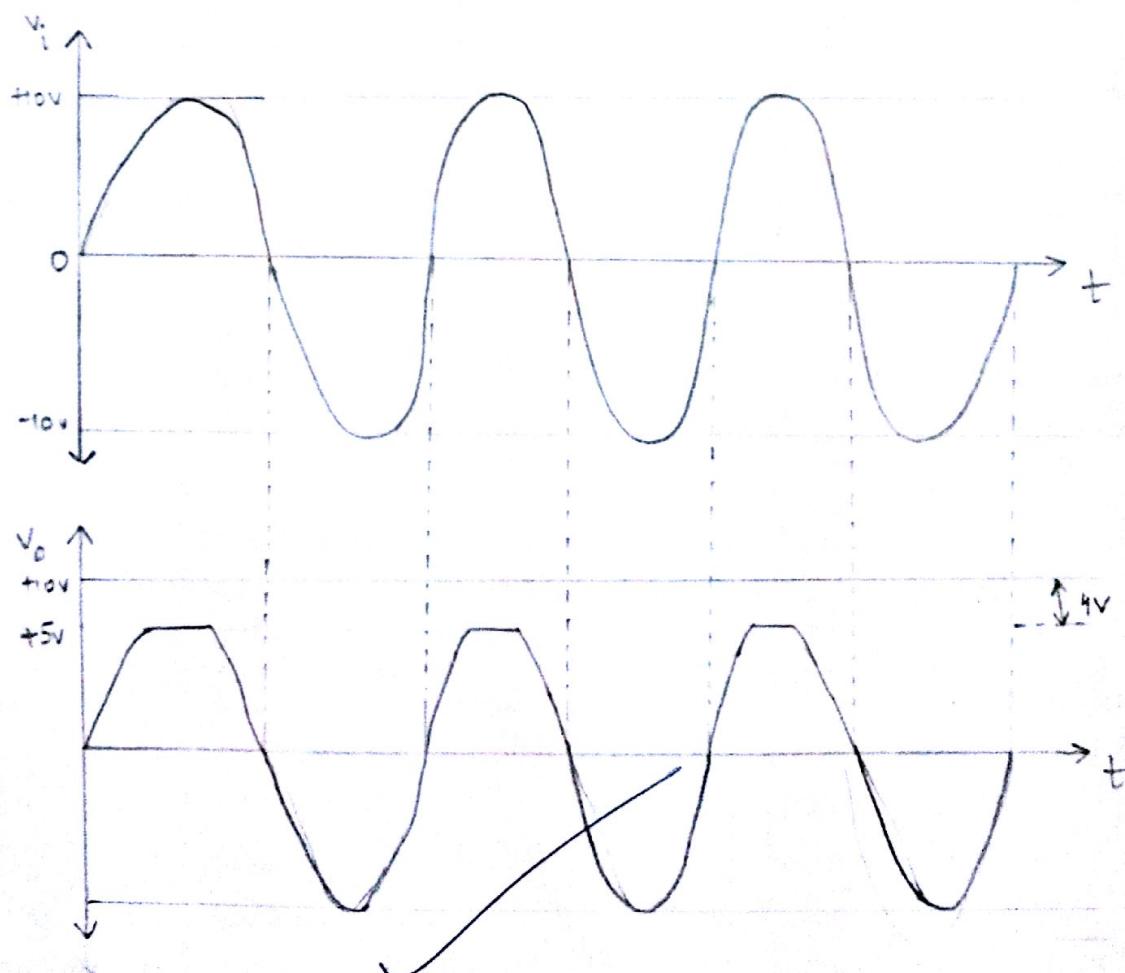

C :-

b) Positive clipper;

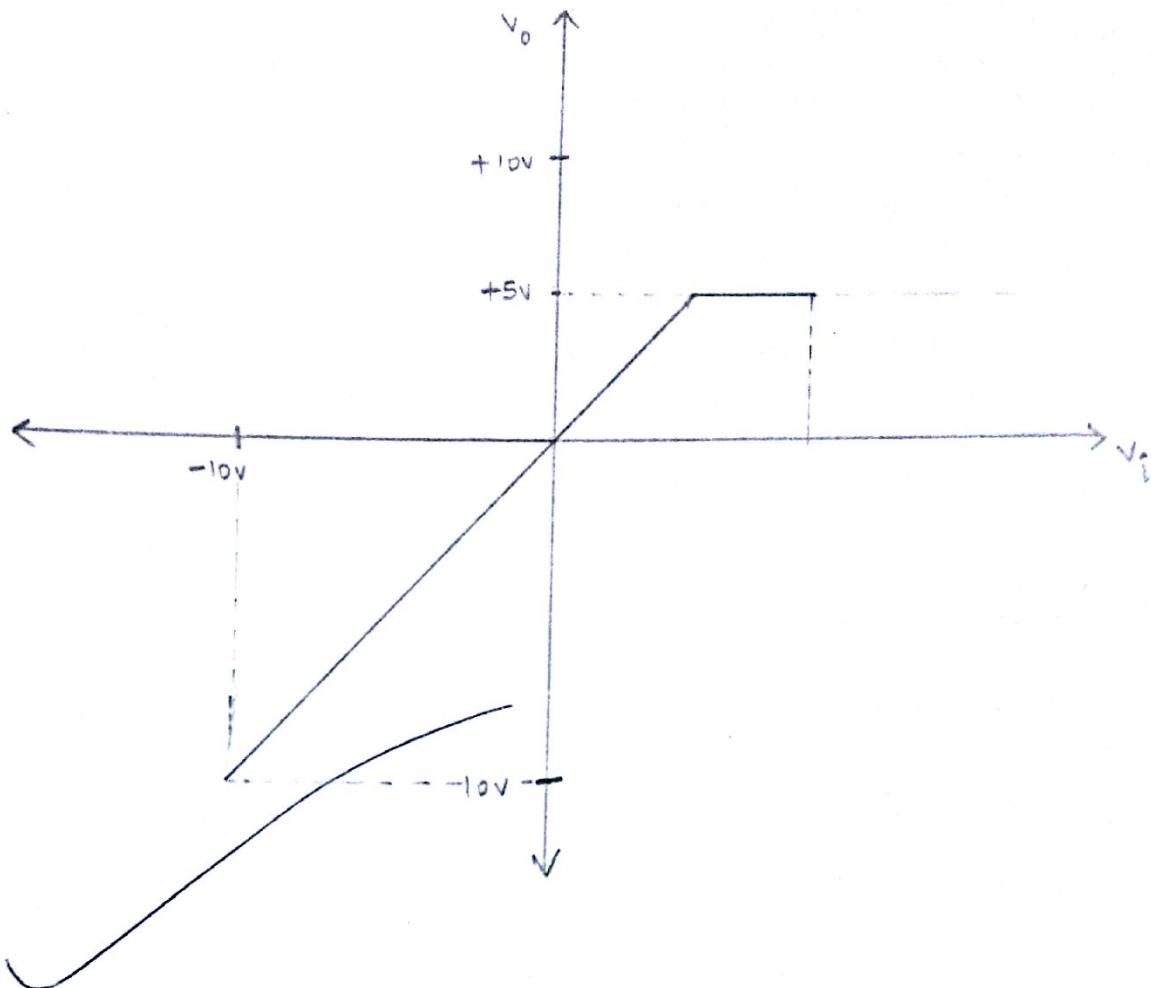

Hijdar,
10/02/2016

EXPT. No. 4 : DIODE CIRCUITS

OBJECTIVES : Design and analysis of half wave rectifier and clipping circuits.

MATERIALS REQUIRED

- Breadboard
- Equipment : Function Generator, Oscilloscope
- Components :
 - Diode : One: Type 1N4007 (Diode voltage drop $V_D = 0.7V$)
 - Zener Diode : One: (Zener voltage $V_Z = 3.9 V$)
 - Resistance : Four: 56Ω , $1 k\Omega$, $2.2 k\Omega$, $4.7 k\Omega$
 - Capacitor : One: $22 \mu F$.

GENERAL GUIDELINES / PREQUATIONS

1. Connect the capacitor with correct polarity. The capacitor being of electrolytic-type, it is polarized, and will be damaged if connected with incorrect polarity. Similarly, confirm the polarity of the diodes before connecting.
2. Keep ground terminals of oscilloscope probes and function generator outputs connected together throughout the experiment.
3. In an oscilloscope, for higher precision, increase vertical sensitivity (i.e. lower value of volt/div), especially while measuring small amplitude levels (e.g. ripple voltage). You may need to switch to ac coupling while doing so.

PART A : HALF - WAVE RECTIFIER WITHOUT FILTER

1. Set the function generator to obtain 10 V peak-to-peak sine wave at 500 Hz frequency. Do not connect any circuit to the function generator. Keep dc offset equal to 0. Observe the function generator output on the oscilloscope and verify sine wave generation.
2. Set up the circuit as shown in Fig. 2.1(a) without the capacitor C, taking $R_L = 2.2 k\Omega$.
3. Now, connect the function generator to the circuit at points F₁ & F₂ as shown in Fig. 2.1(a).
4. Display V_i and V_o simultaneously on the oscilloscope. Sketch V_i and V_o one below the other with identical time and amplitude axes.

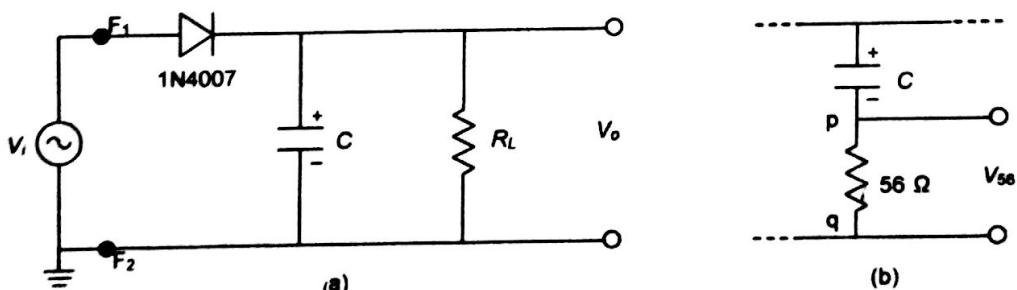


Fig. 2.1 Half-wave rectifier.

PART B : HALF - WAVE RECTIFIER WITH CAPACITOR FILTER

1. Now connect a capacitor $C = 22 \mu F$ in the circuit with correct polarity as shown in Fig. 2.1(a).
2. Display V_i and V_o simultaneously on the oscilloscope. Sketch V_i and V_o overlapping, with the same time and amplitude axes.
3. Measure peak-to-peak ripple voltage on oscilloscope by enlarging V_o to the maximum extent. You may have to put the input coupling in ac mode while doing this measurement. See the guidelines given at the end. Repeat steps 2 and 3 for $R_L = 1 k\Omega$ and $4.7 k\Omega$. Comment on the output waveforms and ripple voltages.
4. Connect a 56Ω resistance in series with C of Fig. 2.1(a) as shown in Fig. 2.1(b). The points across this 56Ω resistor are marked as p and q.

$0.22 \mu F$ $0.2 \mu F$
 $1 k\Omega$ $0.8V$
 $4.7 k\Omega$ $0.12 \mu F$

$\frac{0.6V}{0.83V}$
 $\frac{0.83V}{0.9V}$

Please note that. The resistance 56Ω is chosen small enough not to affect the overall performance of the circuit and at the same time to ensure an appreciable voltage across it. This voltage represents the current flowing through the capacitor.

- Display and sketch V_o and V_{56} (i.e. voltage across 56Ω between 'p' and 'q') one below the other with identical time axes. Mark the ground reference line.

Q.1 : Why is I_C ($=V_{56}/56$), the current through the capacitor, negative for some portion of a cycle? Estimate I_{surge} (positive peak of I_C).

PART C : CLIPPING CIRCUIT - POSITIVE CLIPPER

- Connect the circuit as shown in Fig. 2.2 with $R = 2.2 \text{ k}\Omega$.
- Set the function generator to get 20 V peak-to-peak sine wave at 500 Hz frequency. Observe the function generator output on the oscilloscope and verify sine wave generation.
- Connect the function generator output to the circuit as shown in Fig. 2.2.
- Display and sketch V_i and V_o one below the other with identical time and amplitude axes.
- Superimpose the two waveforms V_i and V_o and observe.
- Set the oscilloscope in X-Y mode (V_i to Ch2 : X-input and V_o to Ch1 : Y-input) and sketch V_o versus V_i with equal x and y scales. Label the graph and ticks on the axes.

Q. 2 : Draw the circuit diagrams for : (a) -ve clipper
(b) +ve and -ve clipper

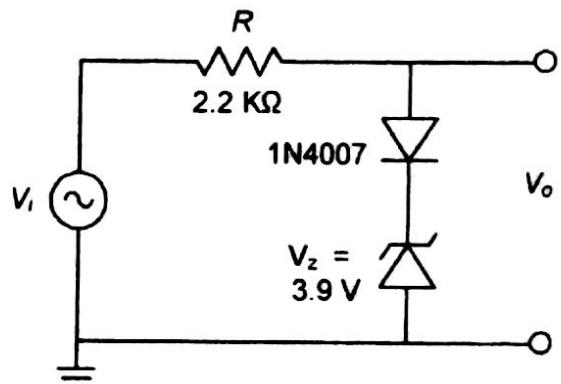


Fig. 2.2 Positive clipper

Pre observation reading:

- (a) Draw the expected waveforms at – (i) Step no. 4 of PART A,
(ii) Step no. 2 of PART B and
(iii) Step no. 4 of PART C.