

(2.5)


for 2

Regular Session & GROUP :	Wednesday, Afternoon (L8)
EXPT. NO:	FIVE (5)
DATE OF EXPT:	17/2/2016
STUDENT-1:	K.Y.Ashok (150107027)
STUDENT-2:	K.Indramani (150107028)
TABLE NO:	FOURTEEN (14)

Objectives → Design and analysis of full-Wave rectifier and Zener regulator.


Materials Required → Bread Board, Oscilloscope, Transformer (230V). Diodes (2); Zener diode, Resistance (3); Capacitor.

Circuit Diagrams →

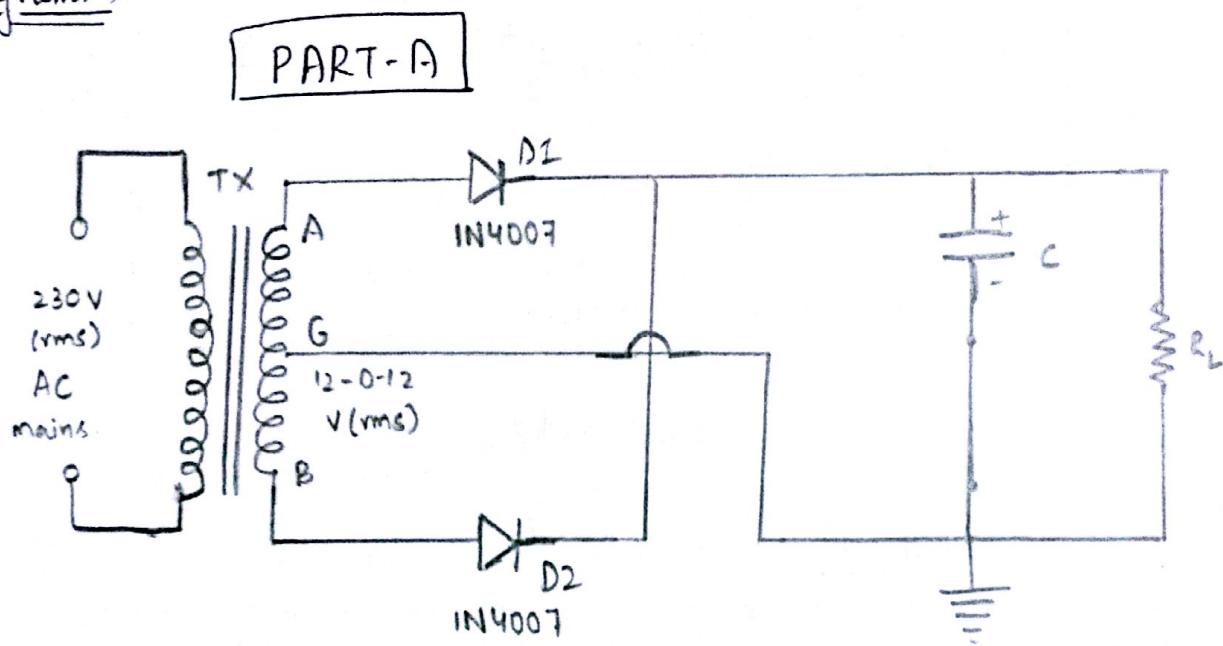

Power Supply using a Centre tapped transformer and full-Wave rectifier.

**PART-B**

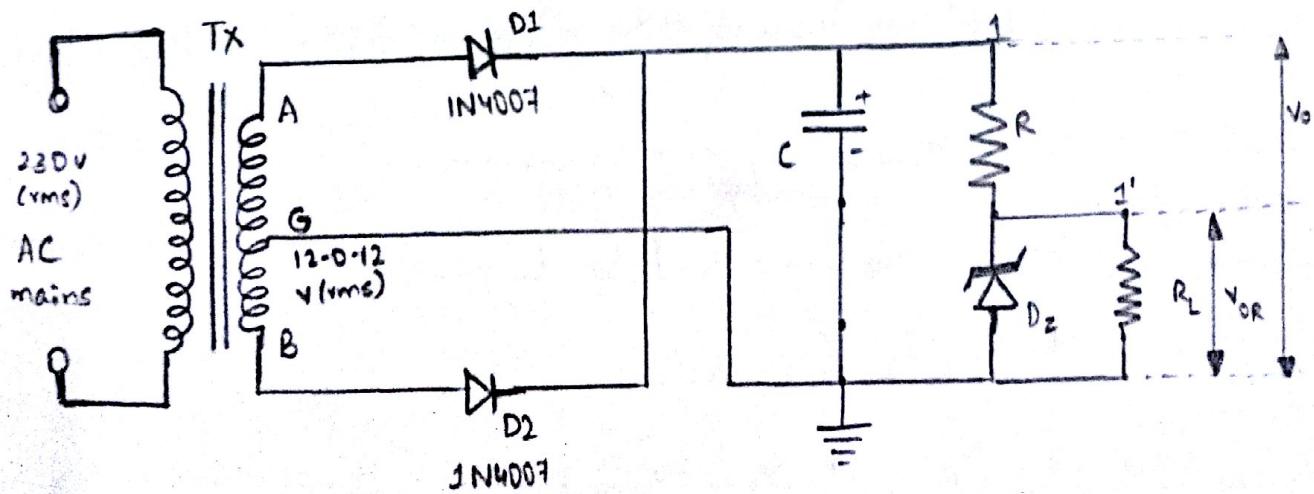

Regulated Power Supply with Zener diode.

## OBSERVATIONS →

### PART-A

Input peak voltage = 18V

For rectifier peak voltage = 18V

Peak to peak ripple voltage of FWR with Capacitor ( $100\mu F$ )

Connected = 1.2V.

Peak to peak voltage at HWR = 2.4V.

$$V_{rms} = \frac{N_o}{\sqrt{2}} = \frac{18}{\sqrt{2}} = \underline{\underline{12.72V}}$$

$$\text{Ripple frequency (FWR)} = \frac{1}{10ms} = \underline{\underline{100\text{Hz}}}$$

$$\text{Ripple frequency (HWR)} = \frac{1}{21ms} = \underline{\underline{47.6\text{Hz}}}$$

### PART-B

$R_L$	$V_o \text{ max}$	$V_r$	$V_{oR \text{ max}}$	$V_{RR(\text{mv})}$	$V_o \text{ av}$	$V_{oR \text{ av}}$	$I_R$	$I_L$	$I_Z$	$P_Z$	$P_R$	% Reg
$\infty$	15	1.04	6.2	2.4	14.48	6.2	14.46	0	14.46	89.6	209	0
$1k\Omega$	15	1.06	6.2	2.4	14.47	6.2	14.46	6.2	8.26	51.21	119	32%
$220k\Omega$	15	1.25	4	3.8	14.38	5.82	15.2	26.49	11.25	65.47	216	36%

$$\% \text{ Reg} = \left[ \left\{ (V_{oR \text{ av}})_{\text{NO-LOAD}} - (V_{oR \text{ av}})_{\text{LOADED}} \right\} / (V_{oR \text{ av}})_{\text{NO-LOAD}} \right] \times 100$$

$$V_{oav} = V_{oman} - V_r/2$$

$$V_{oR \text{ av}} = V_{oR \text{ max}} - V_{RR}/2 \approx V_{oR \text{ max}}$$

$$P_Z = V_Z I_Z \quad (V_Z = V_{oR \text{ av}})$$

$$P_R = V_R I_R \quad (R = V_{oav} - V_{oR \text{ av}})$$

## ST-Experimental Analysis:

- 1) In the 1<sup>st</sup> Part, while taking output voltage reading across  $R_L$  (without capacitor filter) the observed waveform was coming out in the rectified form because the (+ve) terminal of the 1<sup>st</sup> channel of oscilloscope was connected and the (+ve) side of diode rather than an the (-ve) side which gave the required output.
- 2) While finding the ripple voltage, after setting the circuit for capacitor filter, there where difference between peak-to-peak voltage of the wave because the (R<sub>O</sub>) was set with 10V/div which was relatively high to observe this ripple voltage) after reducing V/div; the peaks were visible for calculating the voltage difference.

RESULT →

$$\% \text{ Reg. for } R_L = \infty \rightarrow \% \text{ Reg} = \underline{\underline{0\%}}.$$

$$= 1k\Omega \rightarrow \% \text{ Reg} = \underline{\underline{32\%}}$$

$$= 220k\Omega \rightarrow \% \text{ Reg} = \underline{\underline{36\%}}$$

Conclusion →

- 1) The output produced after center-tapping transformers  $V_{AG}$  &  $V_{BG}$  were  $180^\circ$  out of phase.
- 2) There was a difference (a little bit) in the Peak value at  $V_{in} \Delta V_o$  (across R) FWR.
- 3) The ripple frequency at FWR was almost double at HWR.
- 4) Reg was decreased for increasing resistance in given range (Except  $\infty$ ) or loaded ( $\infty$ ).

5) For loaded cases,  $P_R$  was higher for small resistance.

### Precautions :-

- 1) Switch on the main supply to the transformer only after you have made all other connections.
- 2) While making any change in circuit switch the main supply to transformer.
- 3) Connect the capacitor with correct polarity.
- 4) Connect the diode with correct polarity.
- 5) Ground the probes of CRO while measuring the voltage across transformers as it may get charged due to short circuit.
- 6) Adjust the dc level of CRO prior to peaks of the circuit.
- 7) Discharge the capacitor every time as it may gets charging and show wrong peaks in the CRO.

### Questions :-

- 1) The peak amplitude may be different because the centre tap transformer may be unsymmetric and the no. of turns across AG<sub>1</sub> and BG<sub>1</sub> might be different giving two different voltages.
- 2) The ripple voltage was higher for HWR as compared to a FWR.

$$V_{R(p-p)} \text{ for FWR} = \underline{1.2V}$$

$$V_{R(p-p)} \text{ for HWR} = \underline{2.4V}$$

$$\text{Ripple frequency in HWR} = \underline{47.6 \text{ Hz}}$$

$$\text{Ripple frequency in FWR} = \underline{100 \text{ Hz}}$$

We observed poor regulation for some  $J_L$ , because the current through the Zener was less than the minimum current at which the Zener diode breakdown took place. Hence; if cannot maintain a constant voltage, and it doesn't function as a regulator.

5) Given that;

$$I_Z = 5 \text{ mA} \\ (\text{min})$$

$$P_Z = \frac{1}{2} \text{ W} \\ (\text{max})$$

$$V_Z = 6.2 \text{ V}$$

$$I_R = \frac{V_0 - V_Z}{R} = \frac{14 - 6.2}{560} \approx 15.7 \text{ mA.}$$

6) For an even higher  $I_L$ ,  $R \Delta P_L$  are to be further reduced greatly.

$$P_Z(\text{max}) = 0.5 \text{ W} \Rightarrow V_Z I_Z(\text{max}) = 0.5 \text{ W} \Rightarrow I_Z = 80.64 \text{ mA}$$

$$I_R = I_Z \text{ max. (when } I_Z = 0) = 80.64 \text{ mA}$$

$$R = \frac{15 - 6.2}{80.64 \text{ mA}} \Leftarrow \frac{V_0 - V_Z}{R} \Rightarrow 109 \Omega$$

$$I_R = I_Z(\text{min}) + I(\text{max}) \Rightarrow 80.64 - 5 = \underline{\underline{75.64 \text{ mA.}}}$$

7) When  $R_2 \cdot l$ :

$$\left[ P = \frac{V^2}{R} = \frac{8.8 \times 8.8}{109} = \underline{\underline{710.4 \text{ mW}}} \right]$$


8) Yes; We used the correct voltage resistances as the maximum power assumed by resistance was less than power wattage.

}


Take Observations:

PART A →


i) Full-Wave rectifier (FWR)

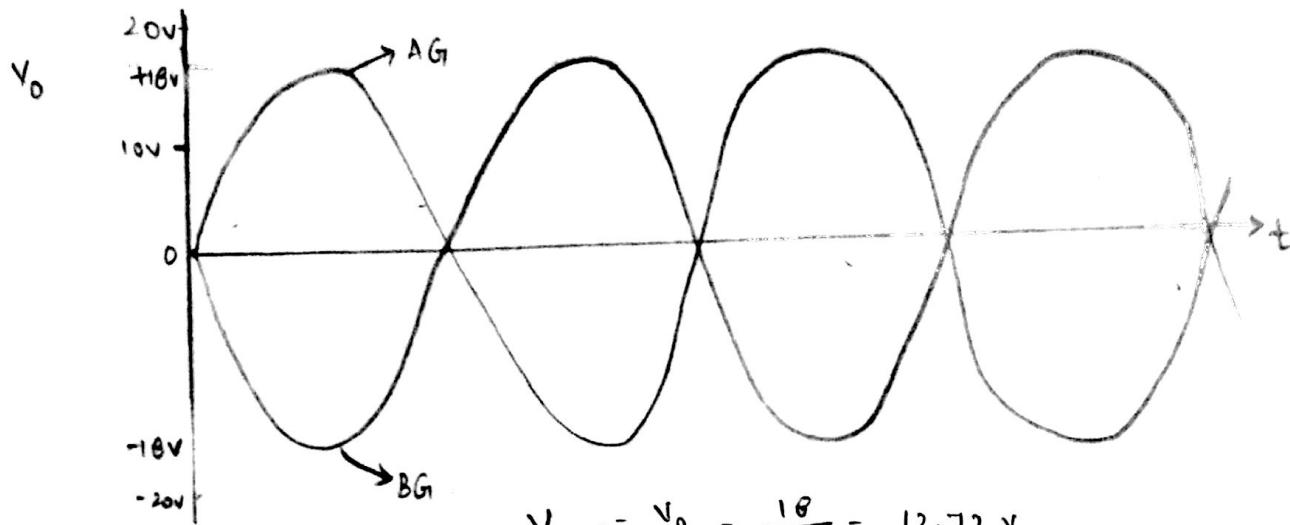

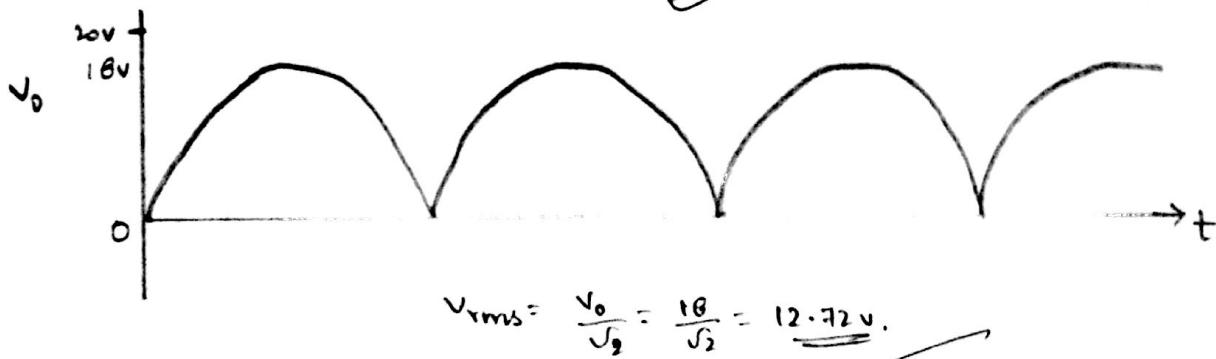$V_o$  Across  $R_L$ ; without Capacitor;



$V_o$  Across  $R_L$  with Capacitor;

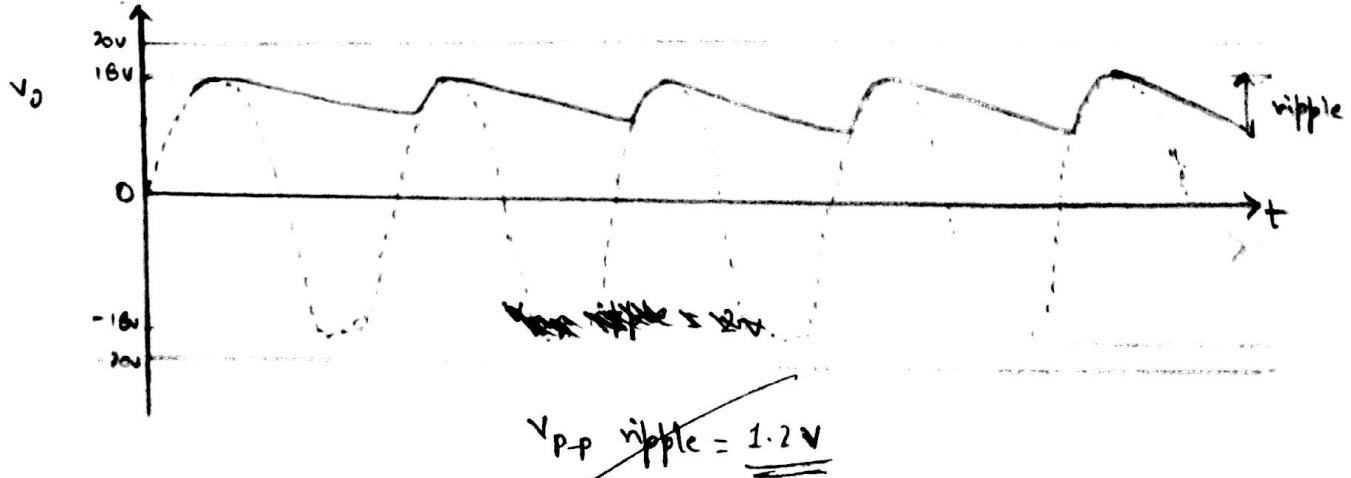

$$\text{Ripple frequency (FWR)} = \frac{1}{\text{Time period}} = \underline{\underline{100 \text{ Hz.}}}$$

ii) Comparison with Half-Wave rectifier (HWR);

a)  $V_{\text{ripple p-p}} \text{ of HWR} = 2.4 \text{ V}$ .


b) ~~Ripple frequency~~  $= \frac{1}{T} = \frac{1}{2\pi} = 47.6 \text{ Hz}$

PART-B:


$R_L$	$V_{o \text{ max}}$	$V_r$	$V_{oR \text{ max}}$	$V_{oR}$	$V_{oav}$	$V_{oRav}$	$I_R$	$I_L$	$I_2$	$P_2$	$P_R$	% Reg
$\infty$	15V	1.04V	6V	2.4mV								
$1k\Omega$	15V	1.06V	6V	2.4mV								
$220\Omega$	15V	1.25V	4V	3.8								

Miydin  
12/02/2016

# 1) Full Wave Rectifier (FWR) →

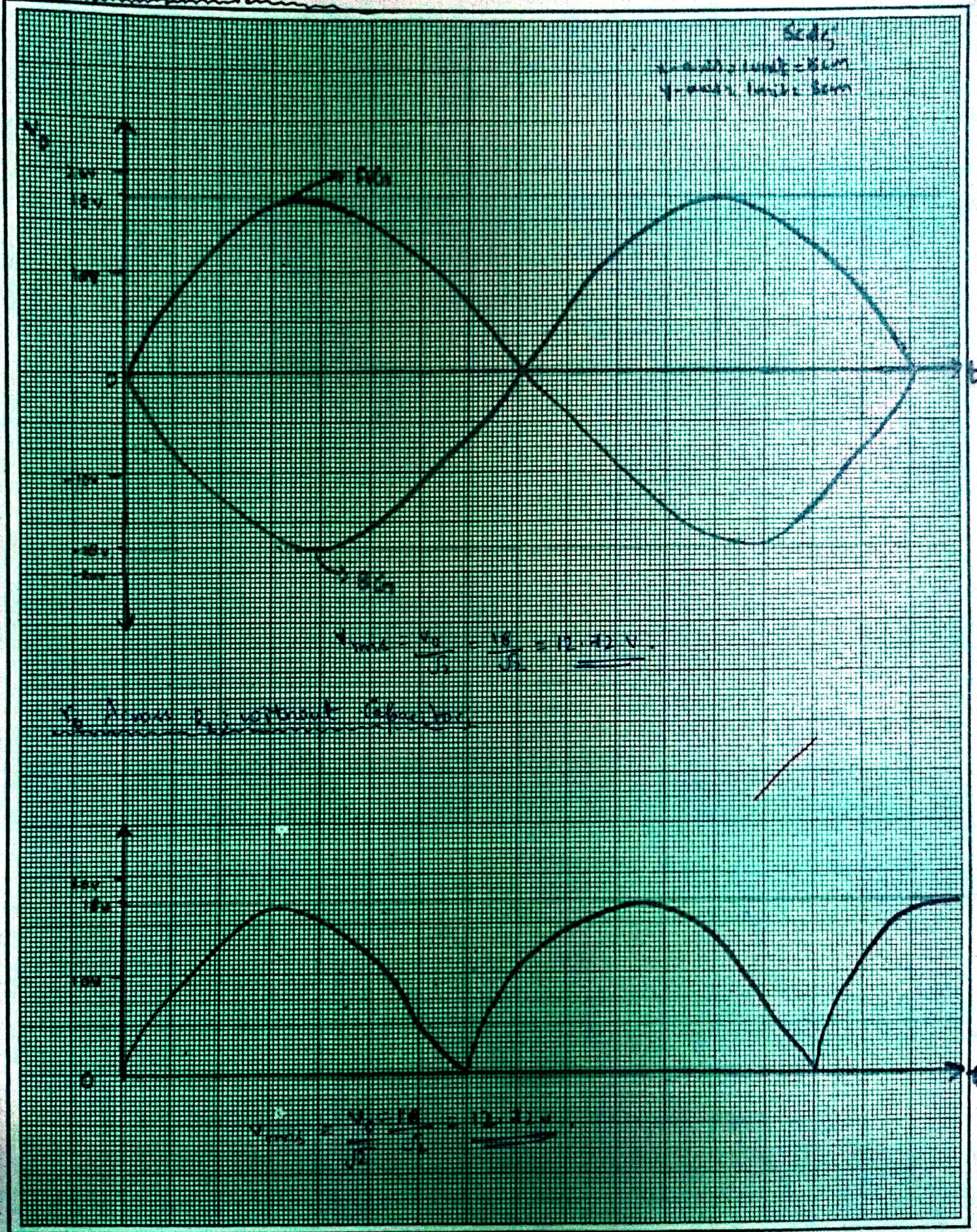

To Across R<sub>1</sub> with Capacitor;

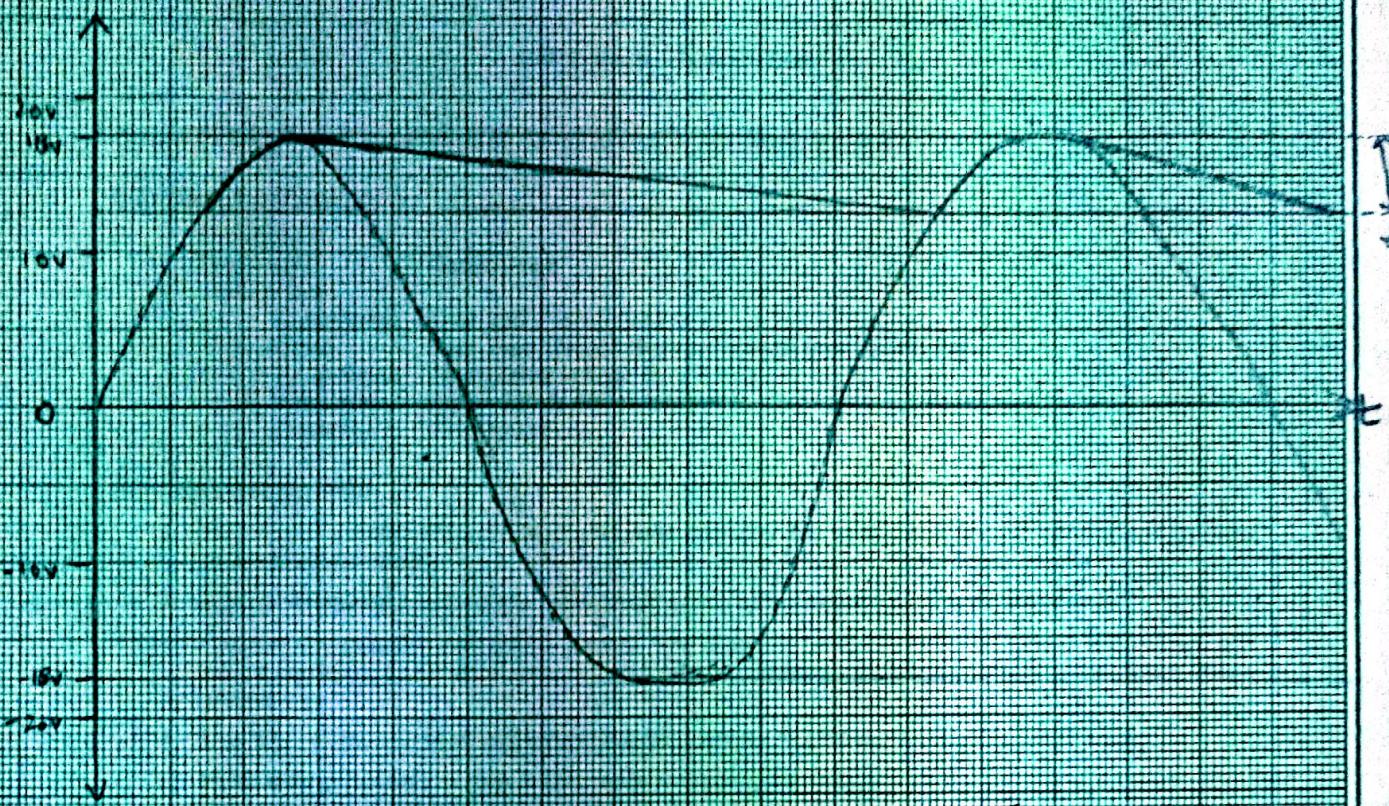

$$V_{pp\text{ Ripple}} = 1.2 \text{ V}$$

$$\text{Ripple frequency (Frok)} = \frac{1}{0.001} = 1000 \text{ Hz}$$

HWR?

### EXPT. No. 5 : POWER SUPPLY

**OBJECTIVES :** Design and analysis of full-wave rectifier and zener regulator.

#### MATERIALS REQUIRED

- Breadboard
- Equipment
- Components
  - : Transformer      One: 230 V to 12-0-12 V
  - : Diode            Two: Type 1N4007 (Forward voltage drop  $V_F = 0.7V$ )
  - : Zener Diode     One: (Zener voltage  $V_Z = 6.2 V$ )
  - : Resistance      Three:  $220 \Omega$ ,  $560 \Omega$ ,  $1 k\Omega$
  - : Capacitor        One:  $100 \mu F$ .

#### GENERAL GUIDELINES

1. Switch on the mains supply to the transformer only after you have made all other connections (in order to avoid electric shock).
2. Also, while making any changes in the circuit, switch off the mains supply to the transformer.
3. Connect the capacitor with correct polarity. The capacitor being of electrolytic type, it is polarized, and will be damaged if connected with incorrect polarity. Similarly, confirm the polarity of the diodes before connecting.
4. Use "line" as the source of triggering in the oscilloscope. Put the oscilloscope in CHOP mode.
5. Never ever ground the probes of CRO while measuring the voltage across transformer as it may get damaged due to short-circuit. Adjust the dc level of CRO prior to connecting the probes to the circuit.

#### PART A : Unregulated Power Supply : Using center tapped Transformer and Full - Wave Rectifier (FWR)

##### i) Full-wave rectifier (FWR)

1. Set up the circuit as shown in Fig. 5.1 without the capacitor C. The transformer TX has rating of 230 V to 12-0-12 V, 1 A. Take  $R_L = 1 k\Omega$ . Connect transformer primary to the mains and switch on the mains. Display the secondary voltages  $V_{AG}$  and  $V_{BG}$  ( $V_{AG}$  to Ch-1,  $V_{BG}$  to Ch-2) on the oscilloscope. Make sure that both the "probe grounds" are connected to the circuit ground. Sketch the waveforms overlapping, with the same time and amplitude axes. They should be  $180^\circ$  out of phase.
2. Display and sketch the full-wave rectified output  $V_o$  across  $R_L$ . Measure the peak voltages in both halves.

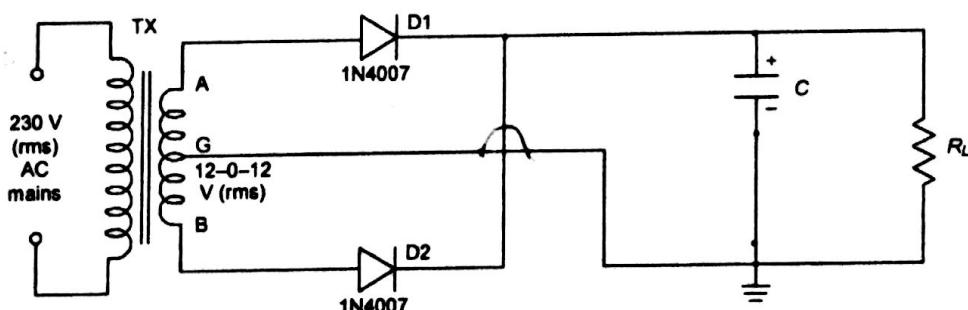


Fig. 5.1 Power supply using a centre tapped transformer and full-wave rectifier.

- Q. 1 : If the peak amplitudes are not equal, what could be the reason?
3. Now connect  $C = 100 \mu F$  as shown in Fig. 5.1. Sketch  $V_o$  and measure  $V_r$  (peak-to-peak ripple voltage). Set the oscilloscope channel to AC coupling and increase vertical sensitivity (decrease V/div) while measuring  $V_r$ .

## II) Comparison with half-wave rectifier (HWR)

1. Remove diode D2. The circuit is now a HWR with C-filter.

2. Compare  $V_o$  values in FWR and HWR.

Q. 2 : What are the ripple frequencies in FWR and HWR?

## PART B : Regulated Power Supply : FULL - WAVE RECTIFIER WITH ZENER REGULATOR

1. Connect a zener diode  $D_z$  with series resistance  $R = 560 \Omega$  as shown in Fig. 5.2. The voltage across  $D_z$  will now be the desired (regulated) output voltage  $V_{oR}$  which will supply current  $I_L$  to the external load  $R_L$ .
2. With  $R_L = \infty$ , using the oscilloscope measure  $V_o \text{ max}$ , the maximum of  $V_o$  (the unregulated DC along with ripple) &  $V_r$  (peak to peak ripple) at point 1 (unregulated output). Similarly obtain  $V_{oR \text{ max}}$ , the maximum of  $V_{oR}$  (the regulated DC along with ripple) &  $V_{rR}$  at point 1' (regulated output). You will find  $V_{rR}$  to be very small, hence you may have to increase the oscilloscope sensitivity suitably.

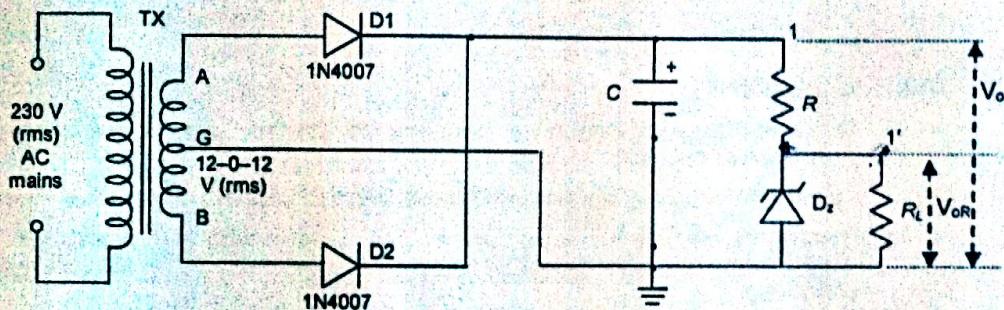


Fig. 5.2 Regulated Power Supply with zener diode.

3. Calculate :  $V_o \text{ av} = V_o \text{ max} - V_r / 2$ , and  $V_{oR \text{ av}} = V_{oR \text{ max}} - V_{rR} / 2 \approx V_{oR \text{ max}}$ . You will notice that the average regulated voltage  $V_{oR \text{ av}} \approx V_{oR \text{ max}}$  (almost equal since  $V_{rR}$  is very small).
4. Compute  $I_R$ ,  $I_Z$ , and  $I_L$  (all average values), and the power dissipations :  $P_Z = V_Z I_Z$ , ( $V_Z = V_{oR \text{ av}}$ ), and  $P_R = V_R I_R$ , ( $V_R$  = voltage across  $R = V_o \text{ av} - V_{oR \text{ av}}$ ).
5. Repeat step 2 and 3 for  $R_L = 1 \text{ k}\Omega$  and  $220 \Omega$ . Enter the measured and calculated values in a tabular form as shown below :

$R_L$	$V_o \text{ max}$	$V_r$	$V_{oR \text{ max}}$	$V_{rR}$	$V_o \text{ av}$	$V_{oR \text{ av}}$	$I_R$	$I_L$	$I_Z$	$P_Z$	$P_R$	%Reg
$\infty$	canc											
$1 \text{ k}\Omega$												
$220 \Omega$												

% Regulation is defined as :

$$\% \text{ Reg} = \left[ \left( (V_{oR \text{ av}})_{\text{NO-LOAD}} - (V_{oR \text{ av}})_{\text{LOADED}} \right) / (V_{oR \text{ av}})_{\text{NO-LOAD}} \right] \times 100$$

Q. 4 : Do you observe poor regulation for some  $I_L$ ? Why does it occur?

Q. 5 : What is the maximum load current the zener regulator (under test) can supply? Given that  $I_{Z \text{ min}} = 5 \text{ mA}$  and the maximum power dissipation in the zener is  $1/2 \text{ W}$ .

Q. 6 : How would you modify the circuit to provide an even higher  $I_L$ ? What is this maximum value?

Q. 7 : What are the wattage ratings of the resistances you will use in the modified circuit for the maximum  $I_L$  value obtained in Q.6? (Standard wattage ratings :  $1/4 \text{ W}$ ,  $1/2 \text{ W}$ ,  $1 \text{ W}$ ,  $2 \text{ W}$ ,  $5 \text{ W}$  etc.)

Q. 8 : Have you used the correct wattage resistances for the circuit under test?